

# Assignment 8

Lakshya J ee19b035

April 22nd, 2021

## Introduction

In this code we try to find the transfer function of the output for various inputs for a high pass and low pass filter. I start by importing these libraries.

```
1 from sympy import *
2 import scipy.signal as sp
3 import matplotlib.pyplot as plt
4 from sympy.utilities.lambdify import lambdify
5 import numpy as np
6 import warnings
```

## Q1

I begin by simulating the Low Pass Filter circuit as given by sir. First I plot the transfer function of the low pass filter with the code as given provided by sir.

Now I attempt to find the time varying response using *scipy.signal.lsim*. I begin by generating a time vector  $t$  and simplify the response  $V_o$ .

Using the following code I extract the numerator and denominator which I then feed into the *scipy.signal.lti* command. This generated a transfer function which can be fed into *scipy.signal.lsim* to generate the time response.

```
1 Vo = Vo.simplify()
2 # Using Poly from the sympy libraray to extract the coefficients of
  numerator and denominator
3 num = Poly(Vo.as_numer_denom()[0], s).all_coeffs()
4 den = Poly(Vo.as_numer_denom()[1], s).all_coeffs()
5 # Converting the extracted coefficients to float type
6 num = np.array(num, dtype = float)
7 den = np.array(den, dtype = float)
8 # using lti to generate the transfer function
9 H = sp.lti(num, den)
```

Here is the plot obtained:

 


Figure 1: Transfer function of low pass filter

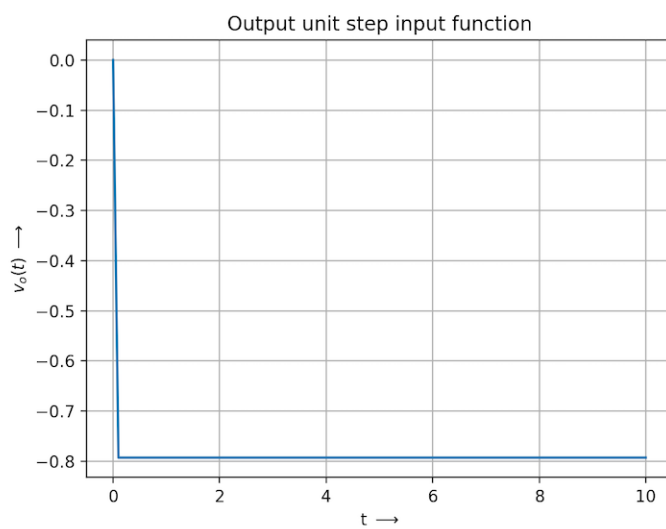


Figure 2: Time varying response to step input

 


Figure 3: Transfer Function of High Pass Filter

## Q2, Q3, Q4, Q5

Now I will solve the circuit for the high pass filter. On analyzing it can be noticed that we can use the same matrix by just replacing all the resistor components with capacitors and vice versa. Here is function implemented to create the high pass filter

```

1 def highpass(R1, R3, C1, C2, G, Vi):
2     s = symbols('s')
3     A = Matrix([[0,0,1,-1/G],[-1/(1+(1/(s*C2*R3))),1,0,0],[0,-G,G
4         ,1],[-s*C1-s*C2-(1/R1),s*C2,0,1/R1]])
5     b = Matrix([0,0,0,Vi*s*C1])
6     V = A.inv()*b
7     return (A, b, V)

```

I will now plot the transfer functions for the various inputs. I do so by multiplying the laplace transforms of the various inputs with the obtained transfer functions.

First I plot the transfer function for a constant input of 1. Now I am plotting I obtain the transfer function for the input  $V_i = \cos(2 * 10^6 \pi t) + \sin(2000 \pi t)$ .

Here is the code for the same:

```

1 f = cos(2e6*np.pi*t) + sin(2000*np.pi*t)
2 vi_L = laplace_transform(f, t, s, noconds=True)
3 A,b,V_ = highpass(10000, 10000, 1e-9, 1e-9, 1.586, vi_L)

```

I pass the laplace transform as the input function for the high pass filter method. This is the plot I obtained:

 


Figure 4: Transfer Function of High Pass Filter for  $V_i = \cos(2 * 10^6 \pi t) + \sin(2000 \pi t)$

Similarly I plot the transfer function for a decaying sinusoid. The decaying sinusoid input I took is  $V_i = \cos(2000 \pi t) * \exp(-0.5 * t)$ .

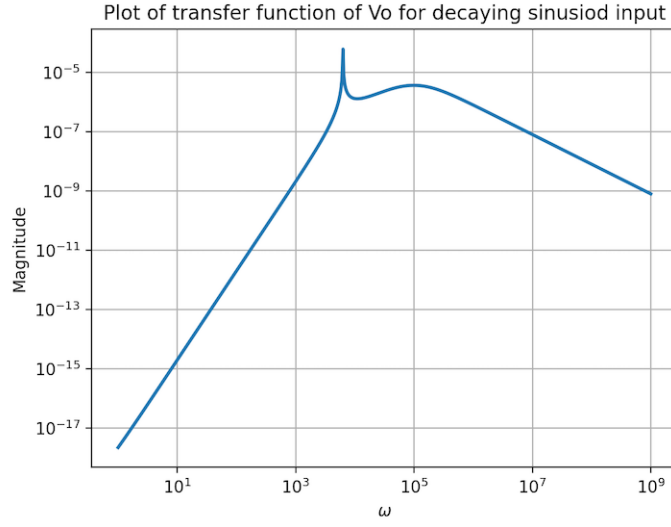


Figure 5: Transfer Function of High Pass Filter for  $V_i = \cos(2000\pi t) * \exp(-0.5 * t)$

Lastly I plot the transfer function for a unit step input. The laplace transform for the step function is  $\frac{1}{s}$ . Here is the plot of the same.

 


Figure 6: Transfer Function of High Pass Filter for  $V_i = u(t)$

After plotting the transfer functions I plot the time varying responses using *scipy.signal.lsim*.

```

1 # Using simplify to make the function easier to read
2 Vo = Vo.simplify()
3 # Using Poly from the sympy library to extract the coefficients of
  numerator and denominator
4 num = Poly(Vo.as_numer_denom()[0], s).all_coeffs()
5 den = Poly(Vo.as_numer_denom()[1], s).all_coeffs()
6 # Converting the extracted coefficients to float type
7 num = np.array(num, dtype = float)
8 den = np.array(den, dtype = float)

```

I use  $V_o$  transfer function obtained from the constant input of 1. Then I find the laplace transformation of each of the inputs and multiply it with the transfer function  $V_o$ , numerator and denominator separately.

```

1 # Finding the laplace transforms of the input function
2 f = cos(2e6*np.pi*t) + sin(2000*np.pi*t)
3 vi_L = laplace_transform(f, t, s, noconds=True)
4 vi_L = vi_L.simplify()
5 # Writing the input as a polynomial
6 num1 = Poly(vi_L.as_numer_denom()[0], s).all_coeffs()
7 den1 = Poly(vi_L.as_numer_denom()[1], s).all_coeffs()
8 # Converting coefficients to float data type
9 num1 = np.poly1d(np.array(num1, dtype = float))
10 den1 = np.poly1d(np.array(den1, dtype = float))
11 # Multiplying the numerators and denominators
12 numf = np.polymul(num, num1)
13 denf = np.polymul(den, den1)
14 # using lti to generate the transfer function

```

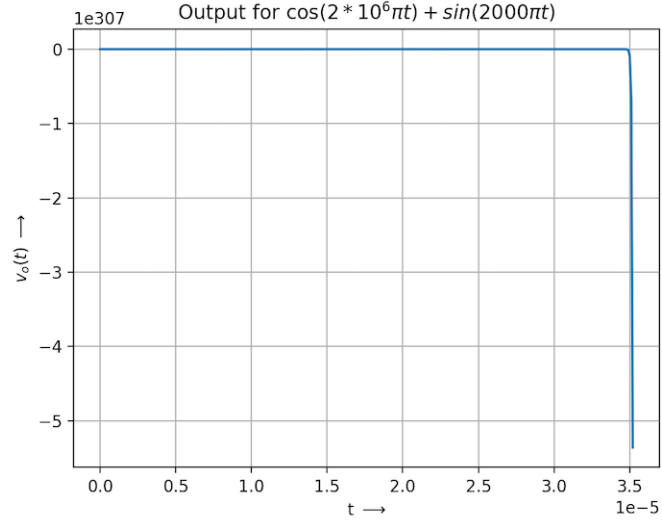


Figure 7: Response for  $V_i = \cos(2 * 10^6 \pi t) + \sin(2000 \pi t)$

```
15 H1 = sp.lti(numf, denf)
```

Hence I obtain the net transfer function after passing it to the *scipy.signal.lti* command. I then use *scipy.signal.lsim* to obtain the time varying response as follows:

```
1 time, y, svec = sp.lsim(H1, np.ones(time.shape), time)
```

I do these for each of the functions and plot the resulting time varying inputs. Here are the plots I obtained.

In this output we see a sudden dip in the output voltage and then it settles to 0. From the transfer function it can be inferred that maximum gain be observed only around  $\omega = 10^5$ . Since the input does not have any such frequency component, the output is observed to be zero.

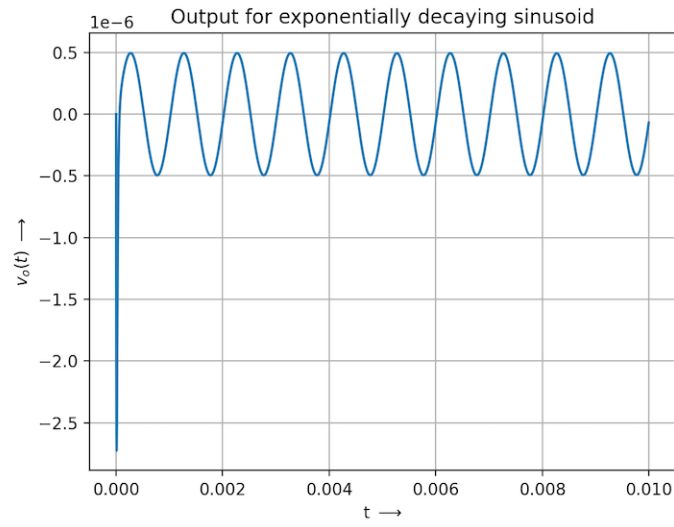


Figure 8: Response for  $V_i = \cos(2000\pi t) * \exp(-0.5 * t)$

 


Figure 9: Response for  $V_i = u(t)$